



Gate-input-signal-improve


2018/07/09 Romeo

Impedance & noise

- **A high impedance circuit is generally more sensitive to noise. this is because a small current (external noise) induced on a high impedance circuit (I times Z) results in higher noise voltage. In contrast, the induced noise on a low Z circuit is generally smaller (I times Z).**
- **You can model a capacitive coupling between a noise source and your circuit with 3 elements.**
 - ▶ a voltage source (the noise source)
 - ▶ a capacitor (the capacitive coupling)
 - ▶ a resistor (the input impedance of your circuit)
- **If the resistor has a small value, you won't get much voltage at the input of your circuit. If the resistor has a big value (high impedance), the voltage will be much higher.**

Reduce impedance & noise


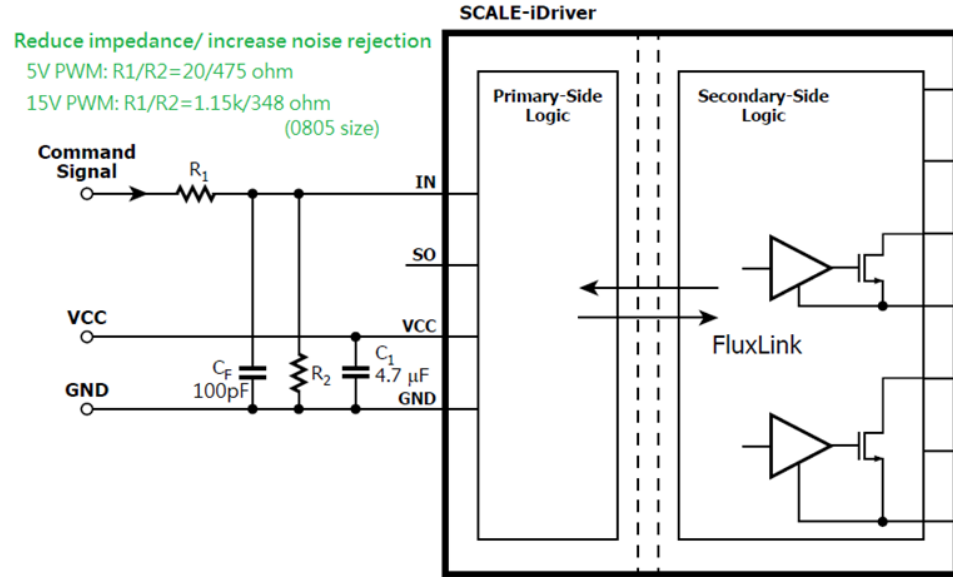
- A opto-coupler driver has 6mA to 10mA LED input current during the IGBT on-state
- Reduce impedance to increase noise rejection capacity as traditional opto-coupler driver circuit For different command signal level
 - ▶ Assume input PWM command is 5V.
 - $I_{in} = 5 / (20 + 475) \sim 10\text{mA}$
 - or
 - ▶ Assume input PWM command is 15V.
 - $I_{in} = 15 / (1.15\text{k} + 348) \sim 10\text{mA}$



Optimize PWM input layout

■ Optimize CP32 and RP32 layout position to close to UP17

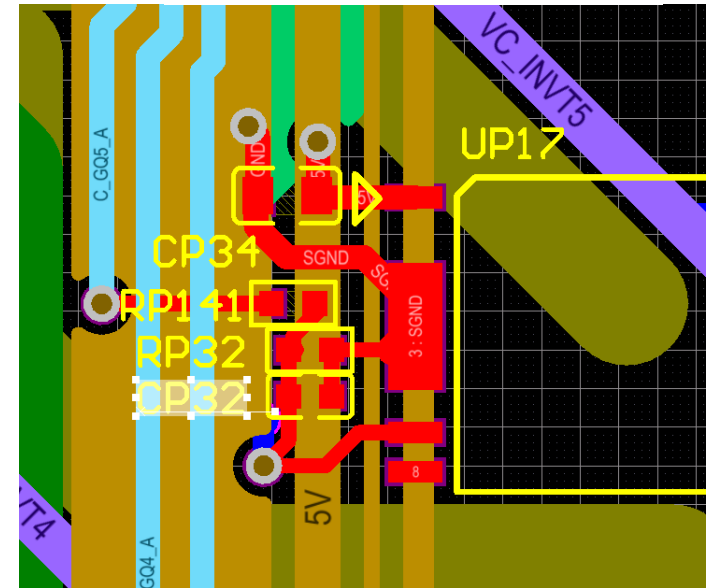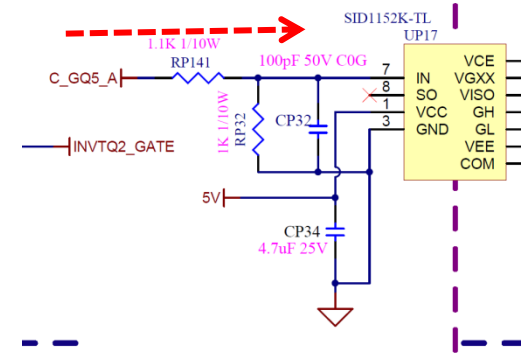- ▶ A voltage divider RP141/RP32 is placed as close as possible to the gate driver (IN pin)
 - PWM input signal should go through RP141 → RP32 → CP32 ; then finally go into the IN pin of Scale-idriver.
 - The minimum distance between the voltage divider RP141/RP32 and the gate driver is essential to avoid inductive coupling on the PCB layout.



Minimum pulse suppression for IN

- Scale-2 gate drivers with electrical interface feature very fast signal propagation delays of typically <math><90\text{ns}</math>. This includes a minimum pulse suppression time of 35ns. To avoid false gate switching caused by potential EMI, the input IN may be equipped with addition filter.

