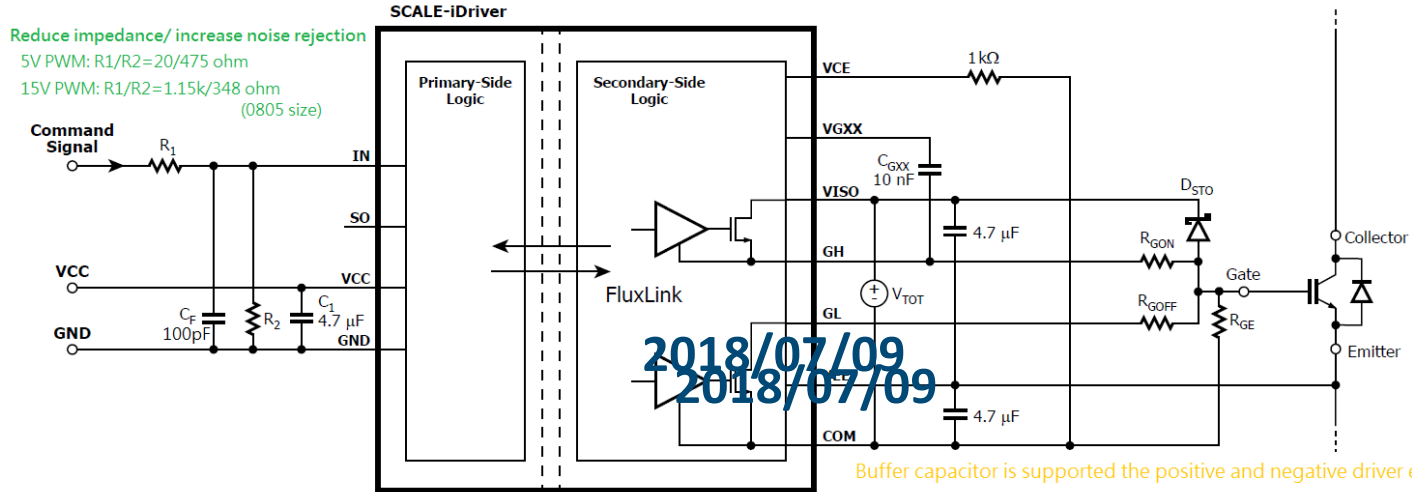




SID1152K circuit layout suggestion


2017/09/25 Romeo

IGBT (No Short circuit protection)




Buffer capacitor is supported the positive and negative driver energy. It is needed to as close each pin as possible. Use 50V capacitor instead of 25V version


COMMON layout suggestion

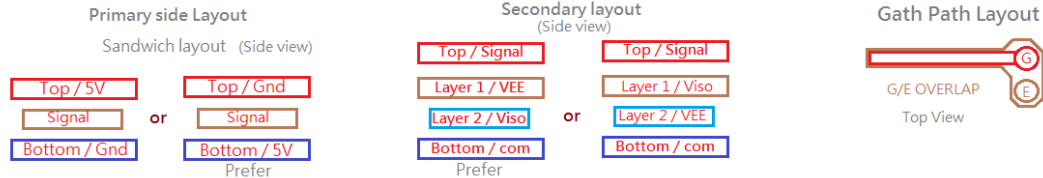

SiC Mosfet (No Short circuit protection)

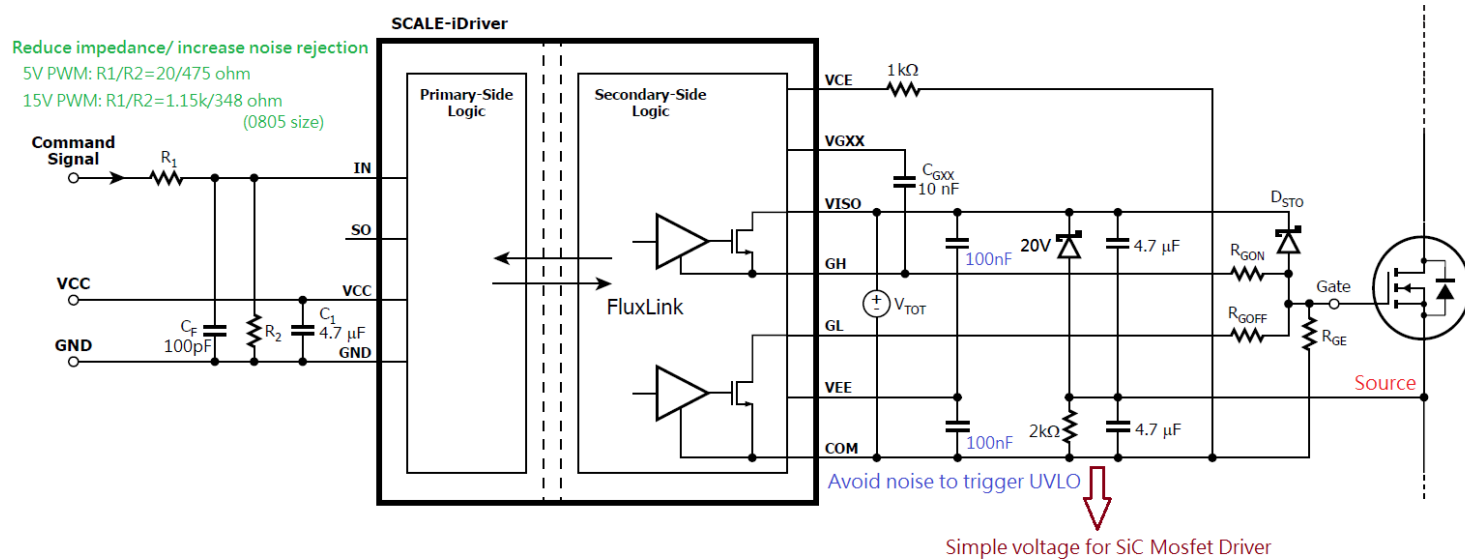

COMMON layout suggestion


 


Remark:

- Schottky diode (D_{STO}) connected between semiconductor gate and VISO pin. The short-circuit current value can be limited to a safe value.
- Since the desaturation detect function is disable, the diode can be omitted to gain more layout size.
- **Disable desaturation function**
 - ▶ V_{CE} is a input pin.
 - ▶ Input pins of an IC are often connected to the gate of a MOS transistor or input of a OPAMP. This input often has extremely high impedance and extremely low capacitance. If left unconnected, the electric field from the outside can easily charge it. The small charge acquired in this way is enough to produce a significant effect on the conduction through the transistor and cause unexpected operation of the IC. So unless otherwise specified, V_{CE} pin should be connected one 1k ohm resistor to the power supply or ground line.

Explain2: Top/Mid-Layer1 Gate & VEE always together(VEE only cross gate loop)

Separate Aux connect

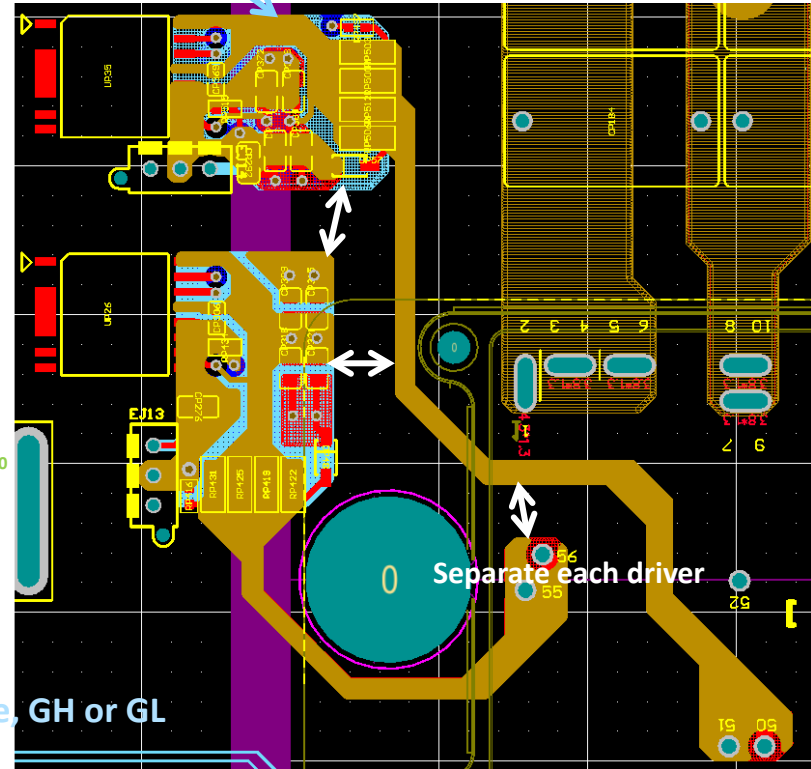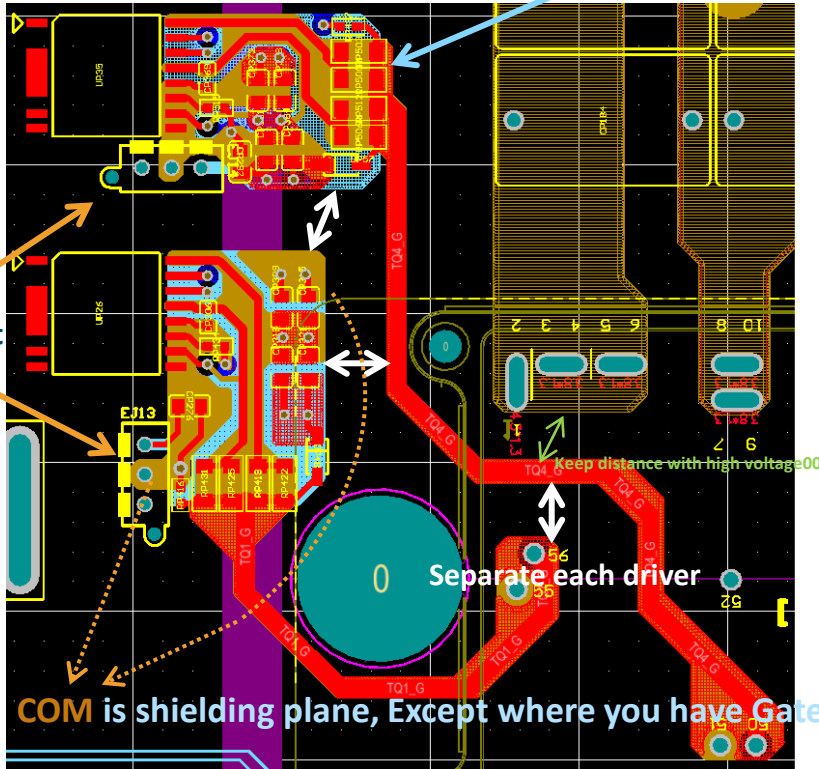

Explain2: Mid-Layer2/Bottom

Viso / COM shielding plane

