


Simple Voltage shifter circuit for SiC MOSFET

2018/04/11 Romeo

Simple Voltage shifter

Clipping with Zener diode

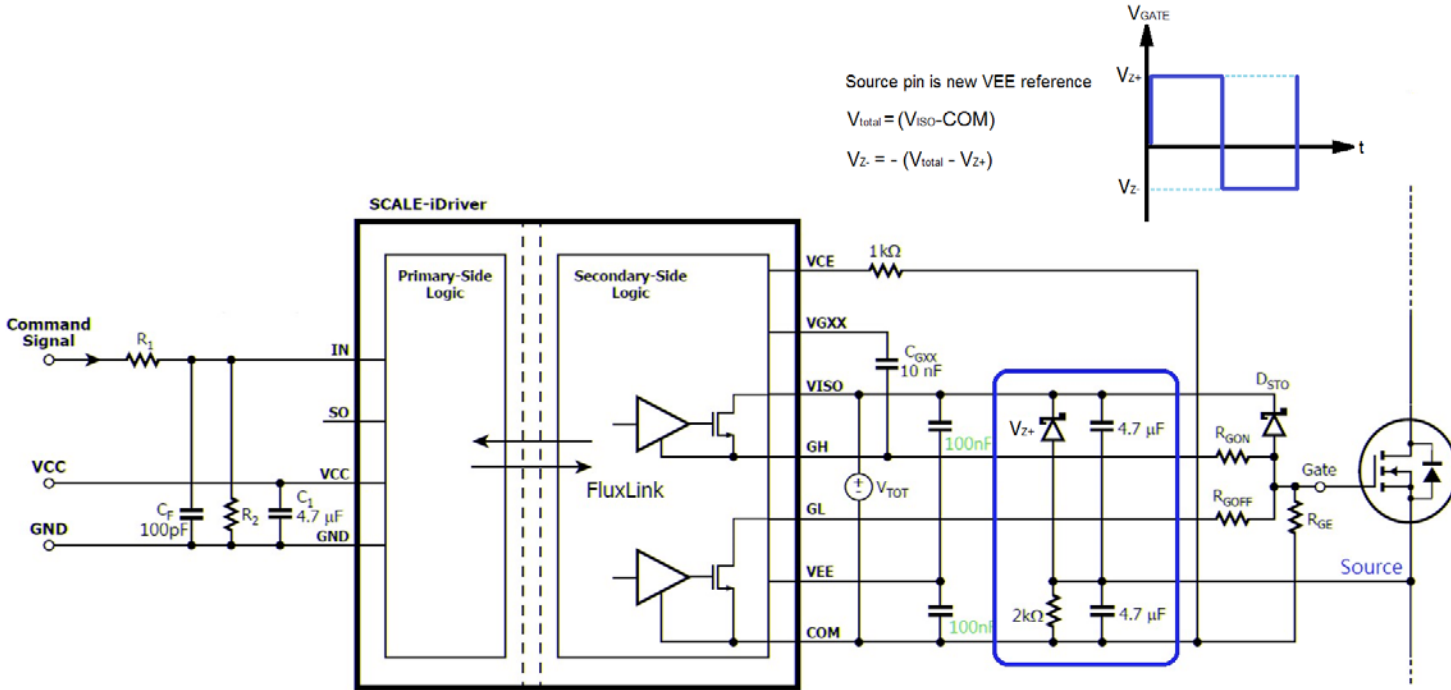
- Deviating gate voltages of $-(V_{TOT}-V_Z) / +V_Z$ instead of -10V/15V



Positive Voltage control


$$V_{TOT} = (V_{ISO}-COM)$$

$$V_{Z-} = -(V_{TOT} - V_Z)$$

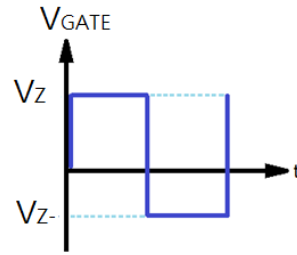

Control Positive voltage, Negative voltage is equal to $-(V_{TOT}-V_Z)$

V_{ISO} to Source will be clamped at V_Z

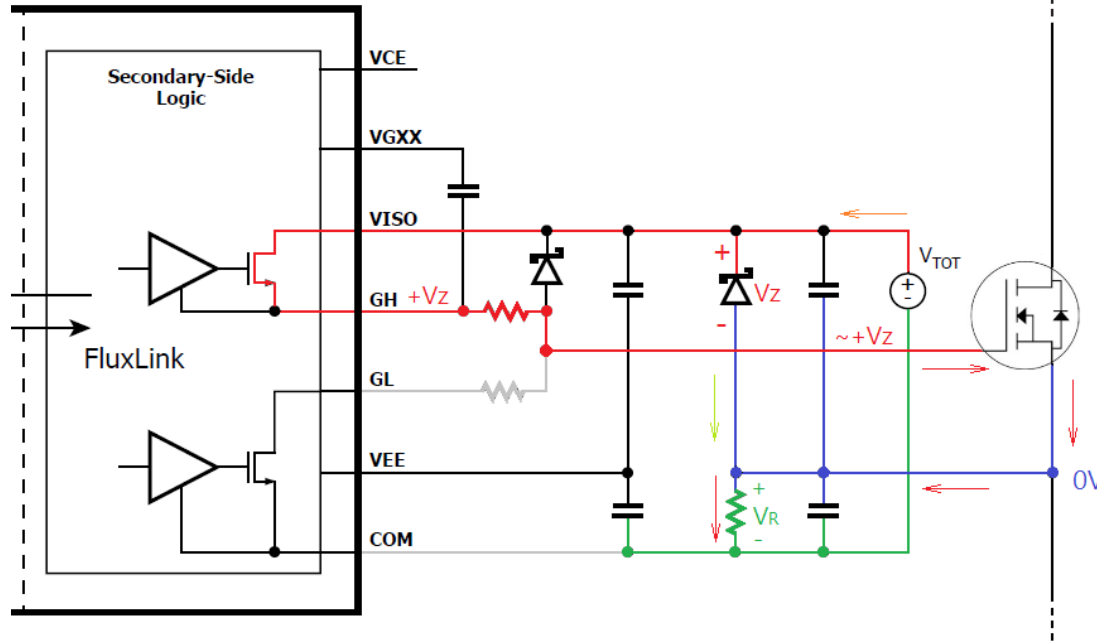



Negative Voltage control

$$V_{TOT} = (V_{ISO}-COM)$$

$$V_{Z+} = V_{TOT} - V_Z$$

Control Negative voltage, Positive voltage is equal to $V_{TOT} - V_Z$

Source to COM will be clamped at V_Z

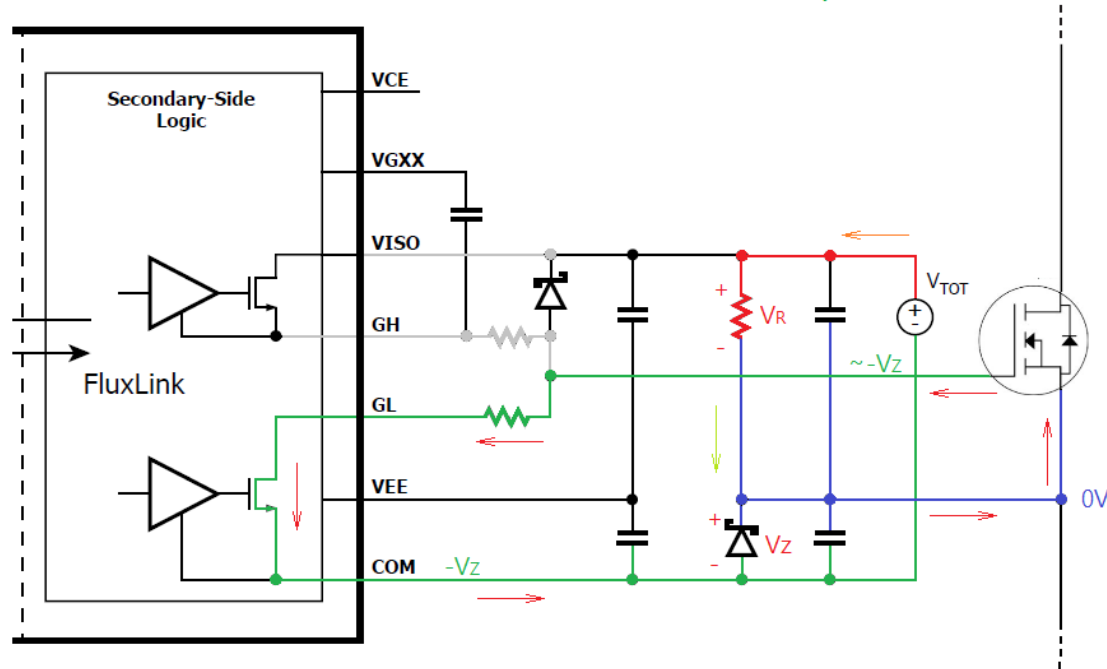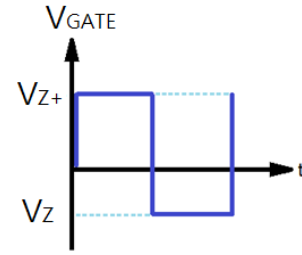

Selection

- **You only can choice One of Positive or Negative control circuit.**
 - ▶ You still need to follow ; $V_{\text{VISO-COM}} = V_{\text{VISO-VEE}} + V_{\text{VEE-COM}}$
 - ▶ Otherwise, you only can choose one to be controlled , positive or negative. Two voltage controlled method working against each other