



Tiny switch BP pin voltage and current limit

March.2019.Romeo

BP Voltage - detection sequence


- On power up BP pin charges to 5.85V
- Then BP pin discharges capacitor with 10 mA current sink.
- Capacitor discharges to 4.9V.
- Time taken to discharge from 5.85V to 4.9V is measured

BP/M Pin Voltage	$V_{BP/M}$	See Note C	5.6	5.85	6.15	V
BP/M Pin Voltage Hysteresis	$V_{BP/MH}$		0.80	0.95	1.20	V
BP/M Pin Shunt Voltage	V_{SHUNT}	$I_{BP} = 2 \text{ mA}$	6.0	6.4	6.7	V

Tiny Switch family

BP Voltage - Regulator & Shunt Voltage Clamp

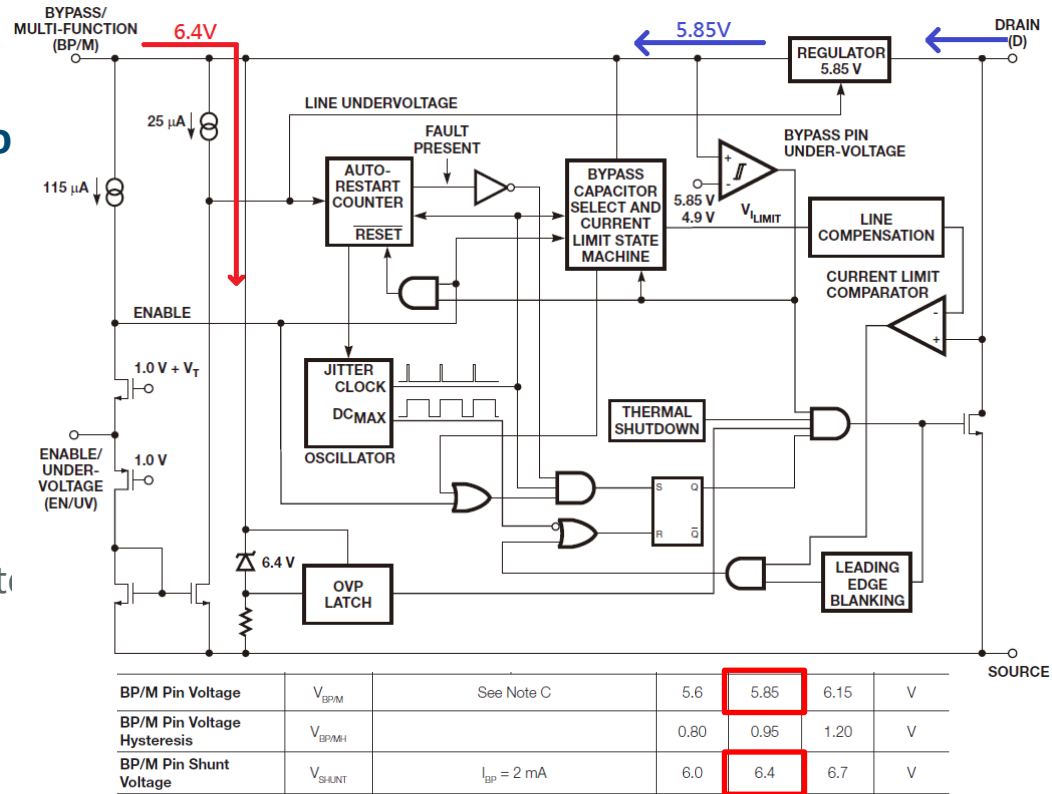
- A current from the voltage on the DRAIN pin to supply 5.85 V regulator
 - ▶ Energy is from Drain pin
- There is a 6.4 V shunt regulator clamping the BP pin at 6.4 V when current is provided to the BP pin through an external resistor.
 - ▶ Energy is from aux winding
 - ▶ Decrease the no-load consumption to well below 50 mW.



External resistor

■ Different device has different supply current request

- ▶ Calculate a suitable resistor to provide a suitable current to achieve the best no-load consumption
- ▶ $R4 = (V_{aux} - V_{BP}) / I_{S2}$

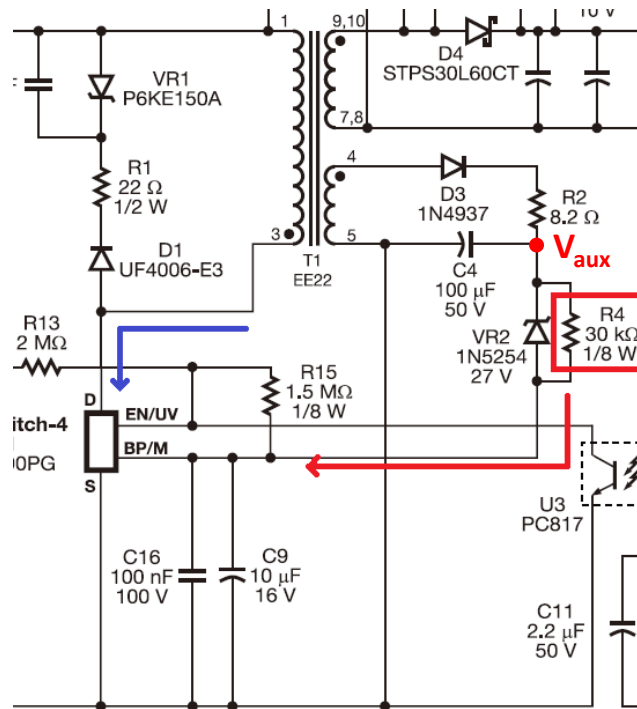

啟動後由外部4-5 Winding 透過R4供電

若無4-5 Winding 則持續由高壓取電

由於IC所需之工作電流為固定的 因此高壓取電時 會產生較多功耗 由4-5 Winding取電可降低功耗

DRAIN Supply Current	I_{S2}	EN/UV Open (MOSFET Switching at f_{OSC}) See Note B	TNY284		μA
			360	400	
			410	440	
			430	470	
			510	550	
			615	650	
			715	800	
			875	930	



BP Voltage

- 開機的時候BP pin電壓會經由Drain pin到內部穩壓器 將BP pin電壓上升到5.85V(typ.) 然後電壓會drop到 $(5.85-0.95)=4.9V$ 再爬升到5.85V.
- 電壓drop的時間是用來設定current limit.
 - ▶ BPP pin電容大小會決定current limit, 0.1uF, 10uF, 1uF三種
- 當輸出電壓上升→aux winding電壓上升→ V_{BPP} pin會透過aux winding電壓經由電阻供電, 電壓會上升到6.4V.


BP/M Pin Voltage	$V_{BP/M}$	See Note C	5.6	5.85	6.15	V
BP/M Pin Voltage Hysteresis	$V_{BP/MH}$		0.80	0.95	1.20	V
BP/M Pin Shunt Voltage	V_{SHUNT}	$I_{BP} = 2 \text{ mA}$	6.0	6.4	6.7	V

BP Voltage Waveform

BP/M Pin Voltage	$V_{BP/M}$	See Note C	5.6	5.85	6.3	V
BP/M Pin Voltage Hysteresis	$V_{BP/MH}$		0.80	0.95	1.20	V
BP/M Pin Shunt Voltage	V_{SHUNT}	$I_{BP} = 2\text{ mA}$	6.0	6.4	6.85	V

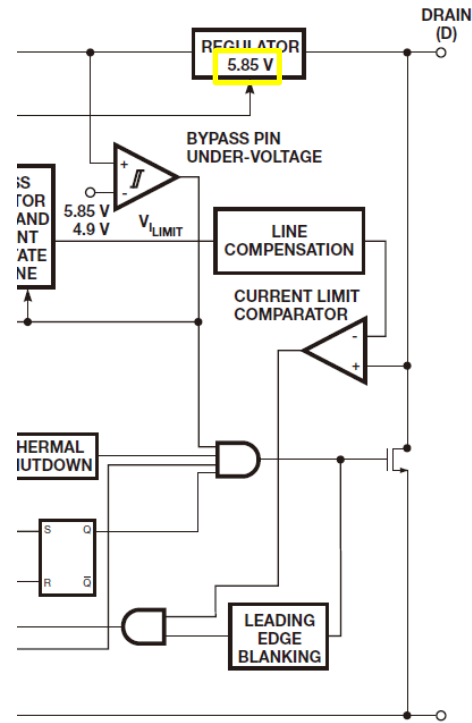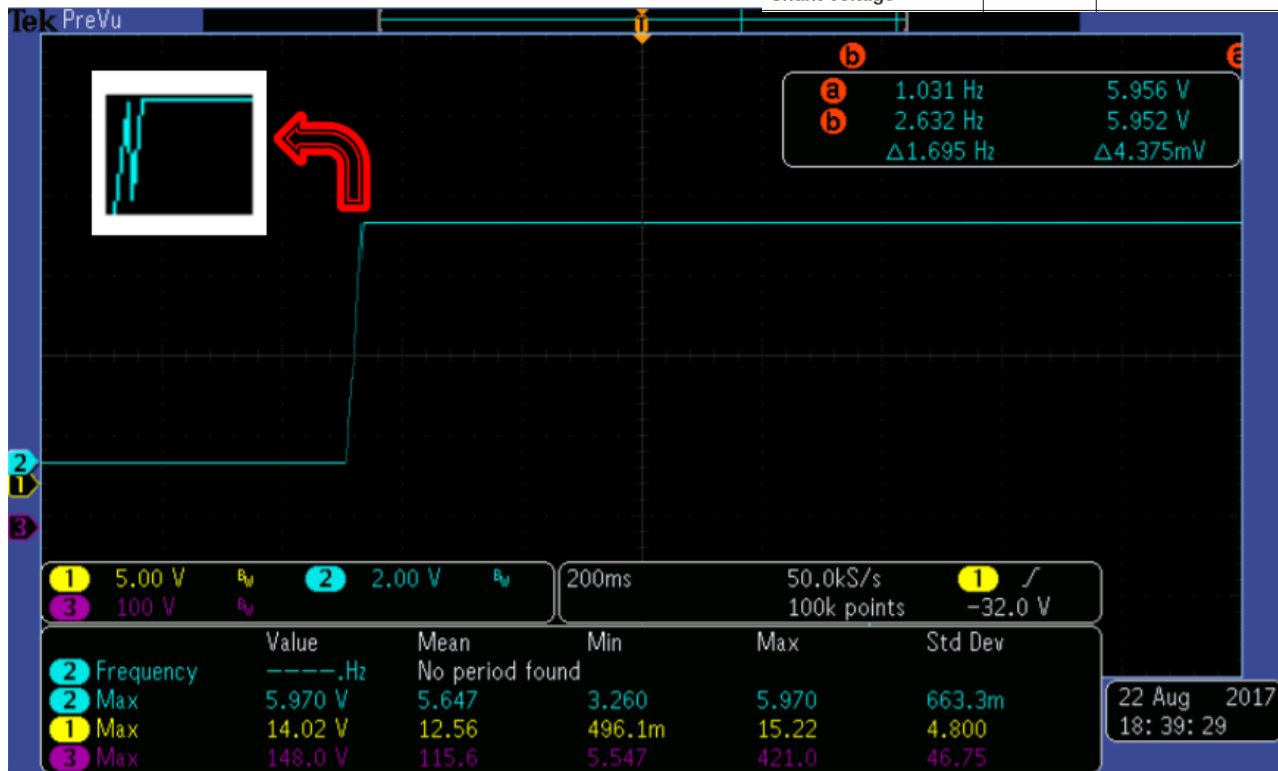

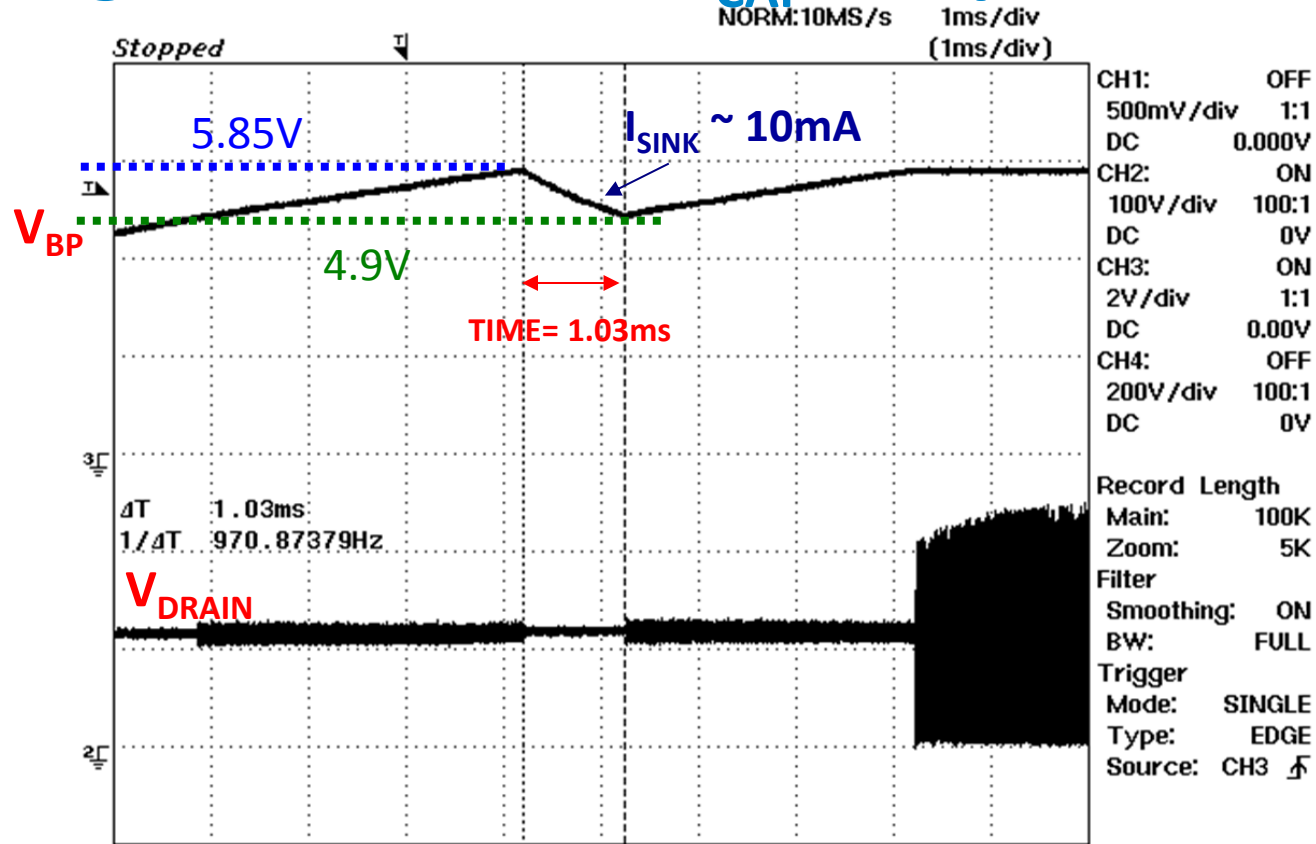BP Voltage Waveform - $BP_{CAP} = 10\mu F$



BP internal timer

BP Capacitor	I_{sink} Time ($I_{\text{sink}} \sim 10 \text{ mA}$)	Internal Timer Cap Detection ($\pm 10\%$)
0.1 μF (Standard I_{Lim})	10 μs	< 30 μs
1 μF (Low I_{Lim})	100 μs	30 $\mu\text{s} < t < 300 \mu\text{s}$
10 μF (Hi I_{Lim})	1 ms	>300 μs